

# **The Linear Systems Problem**

---

## **Electrified**

**Jeffrey Anderson, PhD**  
**Foothill College**  
**April 18, 2015, ©**

# Common Practices in Linear Algebra Education

---

## **Start with Gaussian Elimination**

eg. Anton, Kolman & Hill, Larson, Lay, Leon, Meyer, Olver & Shakiban, Strang

## **Use Implicit Applications**

# **A Better Way?**

---

**Start with Matrix Multiplication**

**Use Explicit Applications**

# A Better Way?

## Four Major Problems

---

**Matrix Multiplication Problem:**

$$A\mathbf{x} = \mathbf{b}$$

**Linear Systems Problem:**

$$A\mathbf{x} = \mathbf{b}$$

**Least Squares Problem:**

$$\min_{\mathbf{x} \in \mathbb{R}^n} \|A\mathbf{x} - \mathbf{b}\|_2$$

**Eigenvalue Problem:**

$$A\mathbf{x} = \lambda\mathbf{x}$$



# Explicit Applications: Linear Systems in Circuit Analysis

---


Linear Systems Problem:

$$Ax = b$$


Use EXPLICIT Application:

Document Camera

# Resistor Ladder: Ideal Circuit Model

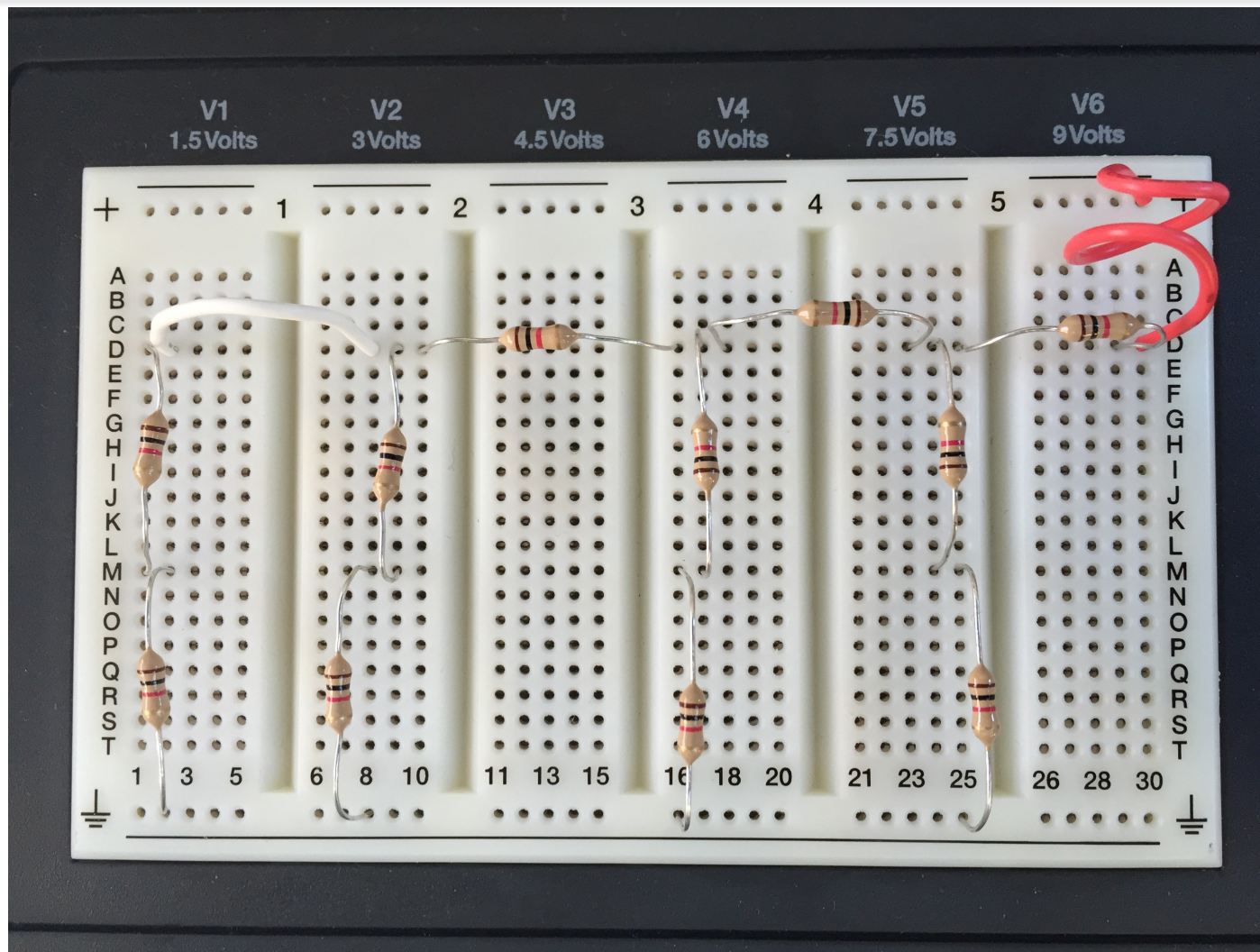


# Resistor Ladder: Ideal Circuit Model

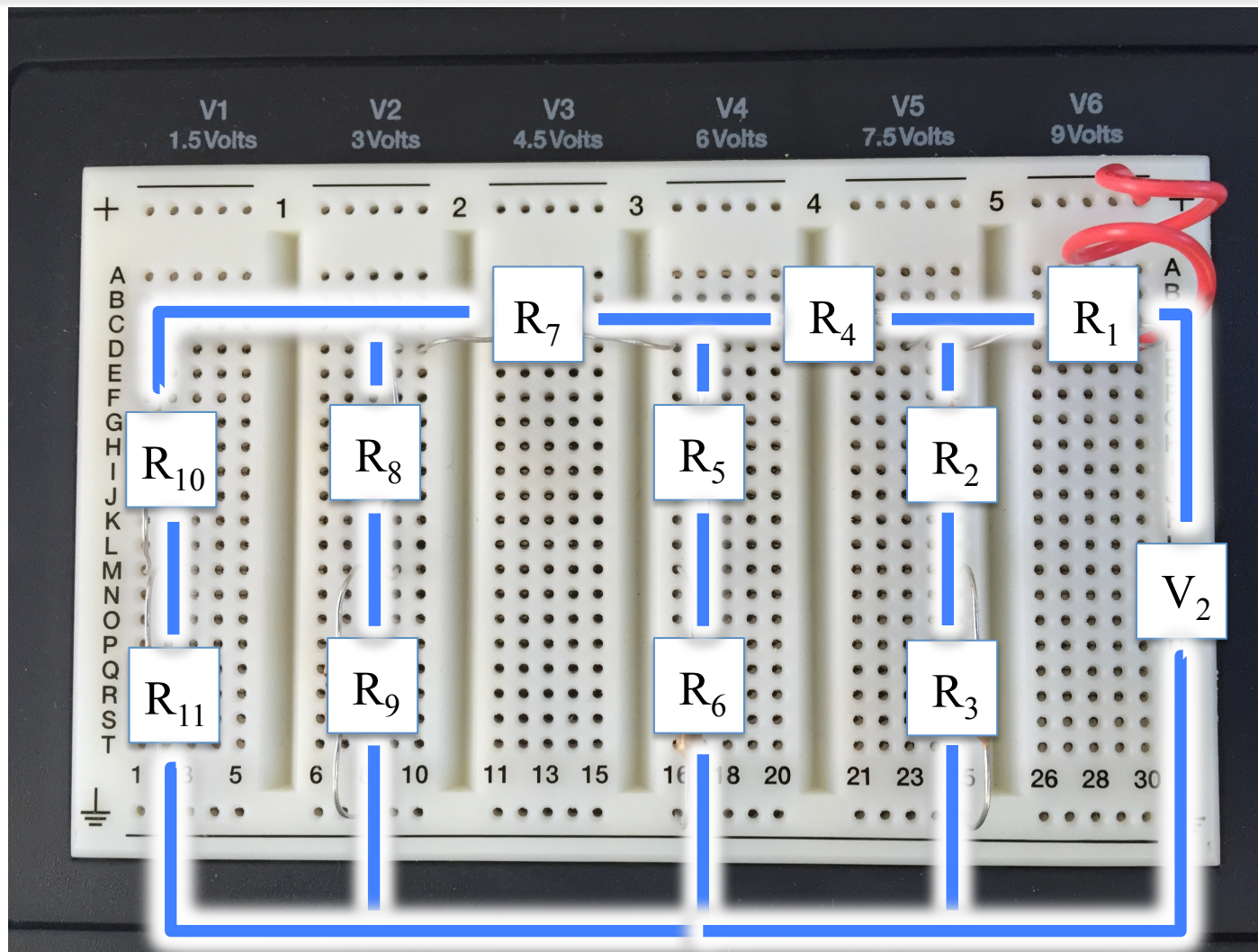


# Resistor Ladders: Directed Graph Model

---

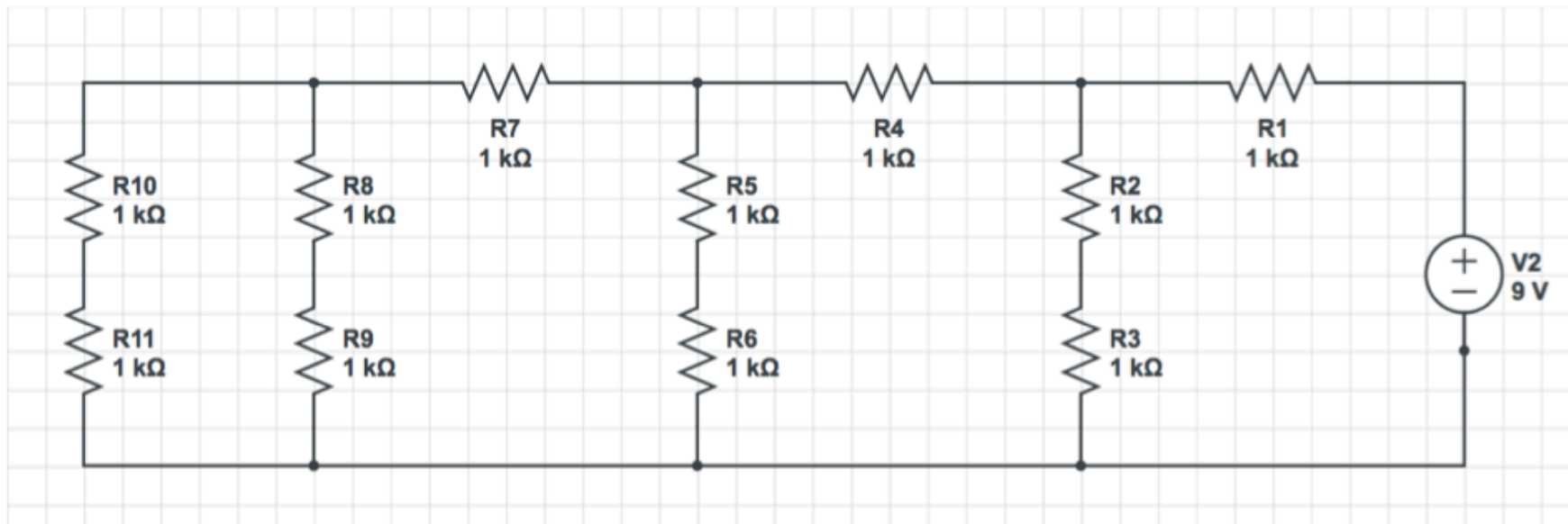





# Resistor Ladders: Directed Graph Model

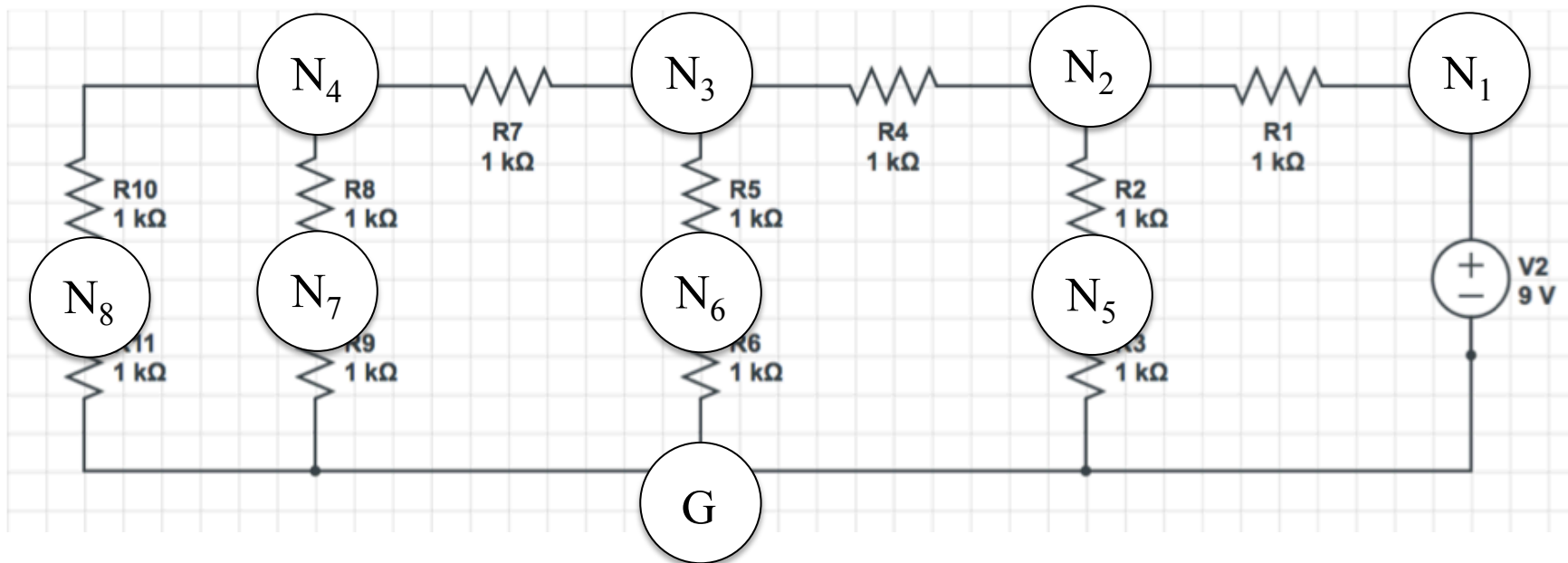

# Resistor Ladders: Directed Graph Model

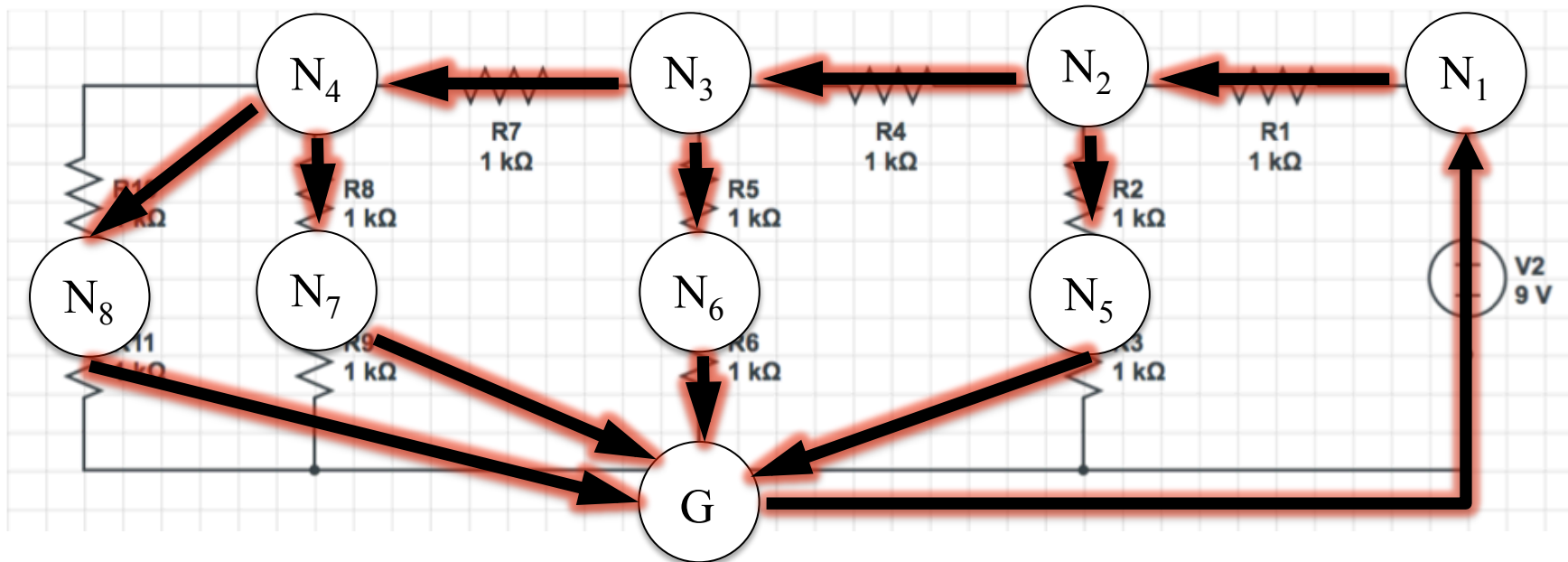
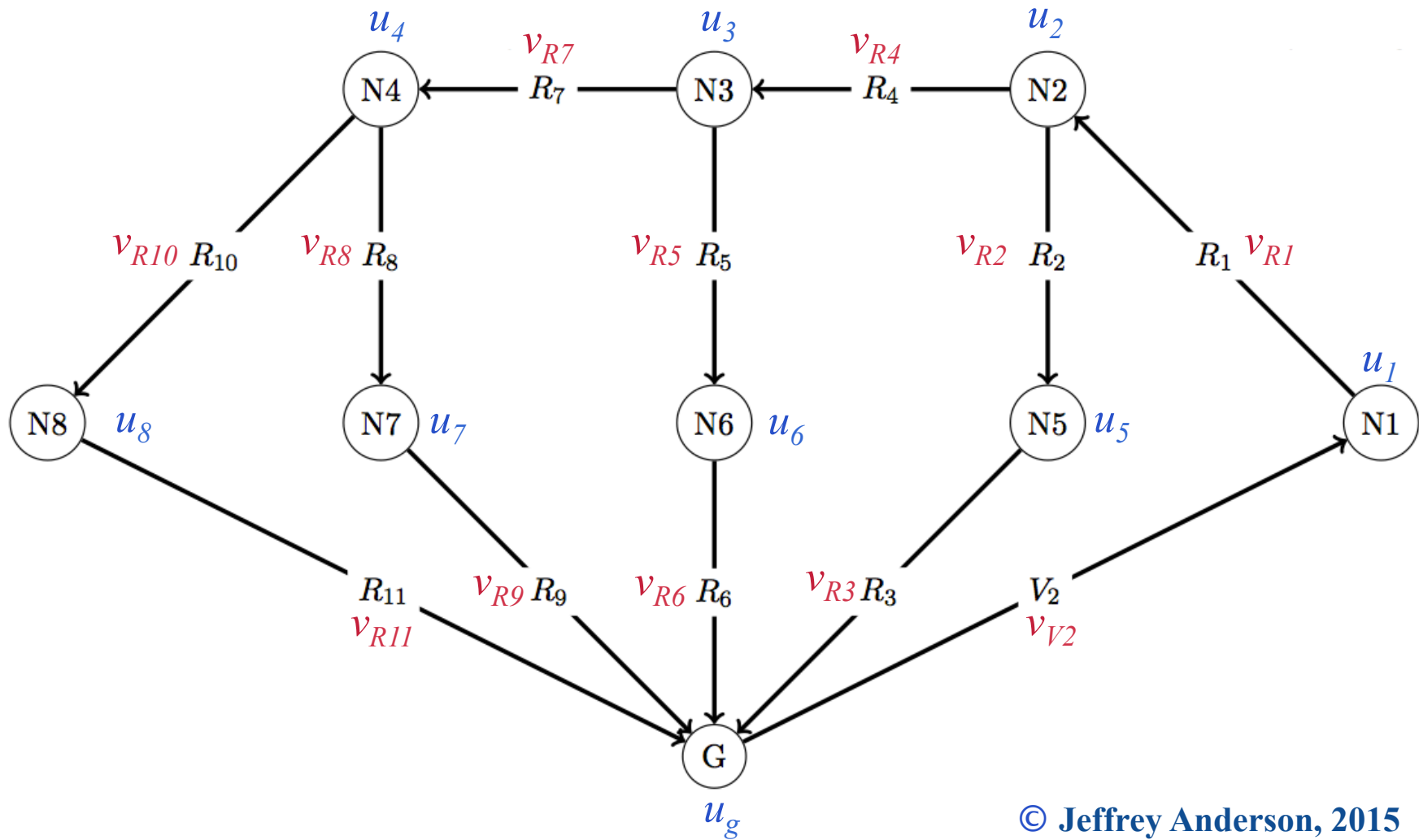
# Resistor Ladders: Voltage Calculations (KVLs)



# Resistor Ladders: KVLs and Matrix Multiplication

$$\begin{bmatrix} v_{V2} \\ v_{R1} \\ v_{R2} \\ v_{R3} \\ v_{R4} \\ v_{R5} \\ v_{R6} \\ v_{R7} \\ v_{R8} \\ v_{R9} \\ v_{R10} \\ v_{R11} \end{bmatrix} = \begin{bmatrix} u_g - u_1 \\ u_1 - u_2 \\ u_2 - u_5 \\ u_5 - u_g \\ u_2 - u_3 \\ u_3 - u_6 \\ u_6 - u_g \\ u_3 - u_4 \\ u_4 - u_7 \\ u_7 - u_g \\ u_4 - u_8 \\ u_8 - u_g \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \\ -1 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} u_g \\ u_1 \\ u_2 \\ u_3 \\ u_4 \\ u_5 \\ u_6 \\ u_7 \\ u_8 \end{bmatrix}$$




# Resistor Ladders: KVLs and Matrix Multiplication

---

$$\begin{bmatrix} v_{R1} \\ v_{R2} \\ v_{R3} \\ v_{R4} \\ v_{R5} \\ v_{R6} \\ v_{R7} \\ v_{R8} \\ v_{R9} \\ v_{R10} \\ v_{R11} \end{bmatrix} = \begin{bmatrix} u_1 - u_2 \\ u_2 - u_5 \\ u_5 - u_g \\ u_2 - u_3 \\ u_3 - u_6 \\ u_6 - u_g \\ u_3 - u_4 \\ u_4 - u_7 \\ u_7 - u_g \\ u_4 - u_8 \\ u_8 \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \\ u_4 \\ u_5 \\ u_6 \\ u_7 \\ u_8 \end{bmatrix}$$

$$\mathbf{v} = \mathbf{A}^T \mathbf{u}$$
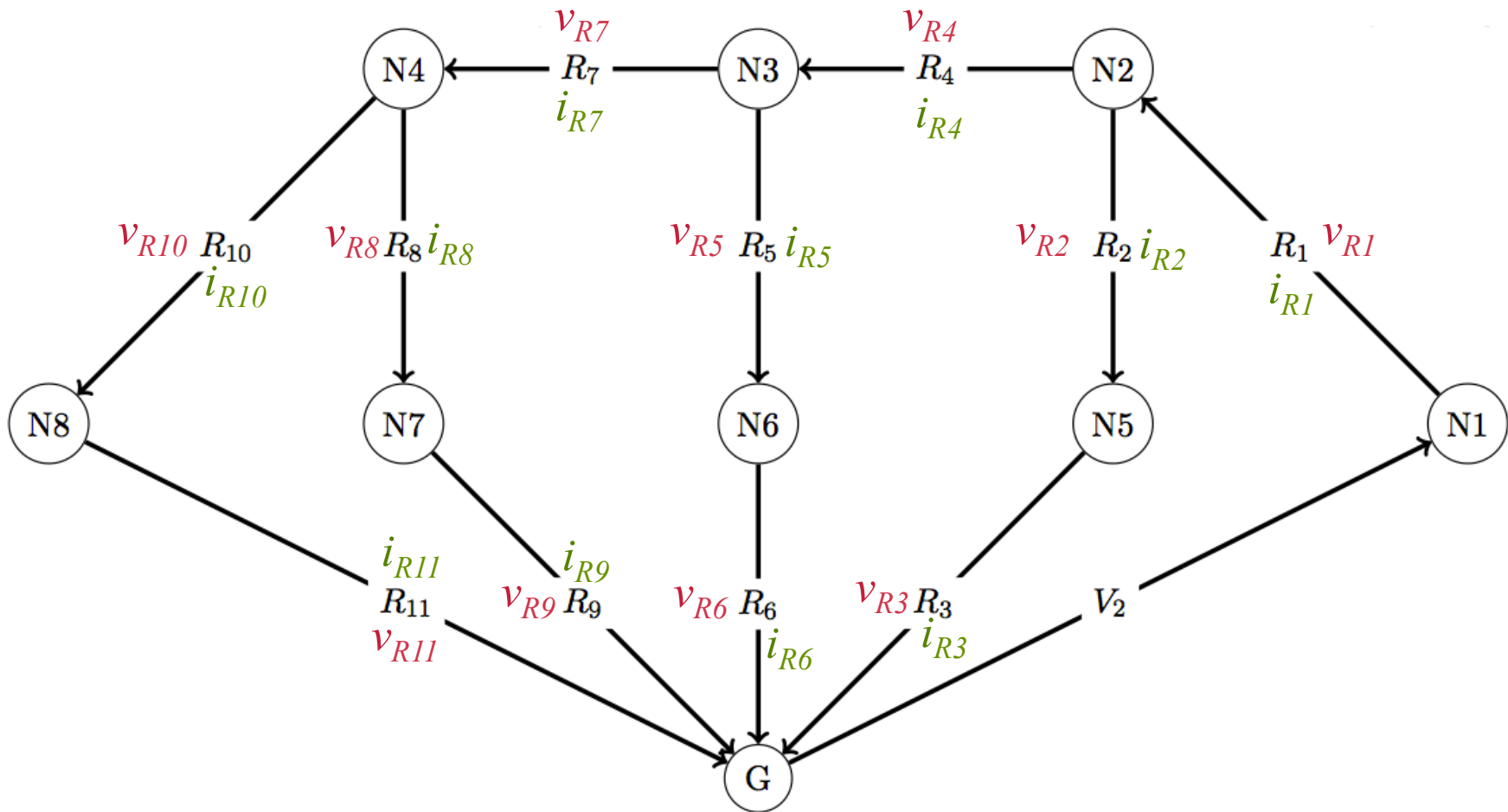
# Resistor Ladders: BRC Calculations (Ohm's Law)




# Resistor Ladders: BCRs and Matrix Multiplication

---

$$\begin{bmatrix} v_{R1} \\ v_{R2} \\ v_{R3} \\ v_{R4} \\ v_{R5} \\ v_{R6} \\ v_{R7} \\ v_{R8} \\ v_{R9} \\ v_{R10} \\ v_{R11} \end{bmatrix} = \begin{bmatrix} R_1 \cdot i_1 \\ R_2 \cdot i_2 \\ R_3 \cdot i_3 \\ R_4 \cdot i_4 \\ R_5 \cdot i_5 \\ R_6 \cdot i_6 \\ R_7 \cdot i_7 \\ R_8 \cdot i_8 \\ R_9 \cdot i_9 \\ R_{10} \cdot i_{10} \\ R_{11} \cdot i_{11} \end{bmatrix} = \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & R_3 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & R_4 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & R_5 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & R_6 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & R_7 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & R_8 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & R_9 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & R_{10} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & R_{11} \end{bmatrix} \begin{bmatrix} i_{R1} \\ i_{R2} \\ i_{R3} \\ i_{R4} \\ i_{R5} \\ i_{R6} \\ i_{R7} \\ i_{R8} \\ i_{R9} \\ i_{R10} \\ i_{R11} \end{bmatrix}$$

$$\mathbf{v} = R\mathbf{i}$$
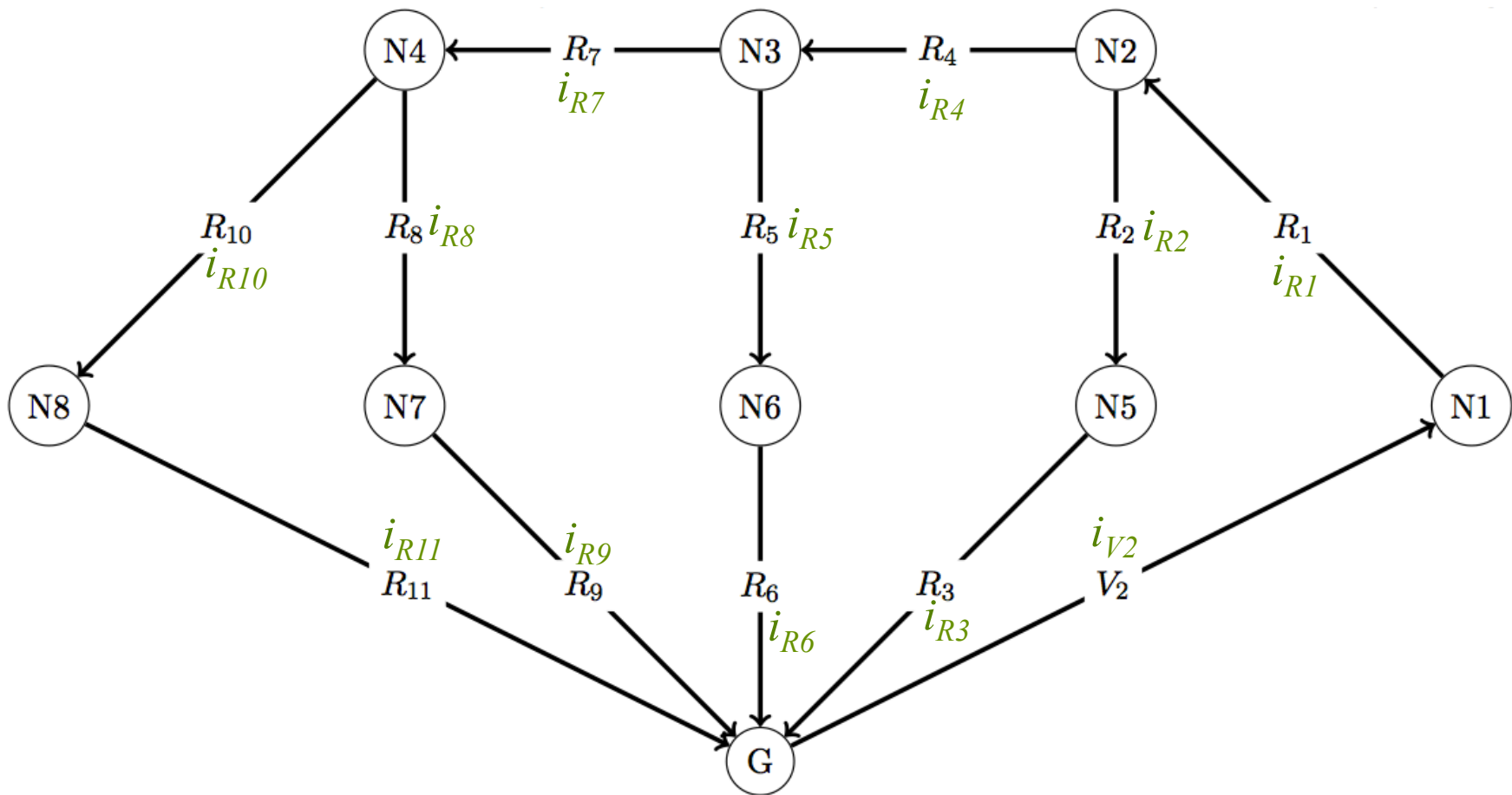
# Resistor Ladders: Current Calculations (KCLs)



# Resistor Ladders: KCLs and Matrix Multiplication

---

$$\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} i_{R1} \\ -i_{R1} + i_{R2} + i_{R4} \\ -i_{R4} + i_{R5} + i_{R7} \\ -i_{R7} + i_{R8} + i_{R10} \\ -i_{R2} + i_{R3} \\ -i_{R5} + i_{R6} \\ -i_{R8} + i_{R9} \\ -i_{R10} + i_{R11} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_{R1} \\ i_{R2} \\ i_{R3} \\ i_{R4} \\ i_{R5} \\ i_{R6} \\ i_{R7} \\ i_{R8} \\ i_{R9} \\ i_{R10} \\ i_{R11} \end{bmatrix}$$

$$\mathbf{0} = \mathbf{A} \mathbf{i}$$

# Resistor Ladders: All Together Now

---

$$\mathbf{v} = A^T \mathbf{u}$$

$$\mathbf{v} = R \mathbf{i}$$

$$\mathbf{0} = A \mathbf{i}$$

$$\mathbf{0} = AR^{-1} A^T \mathbf{u}$$

## Resistor Ladders: All Together Now

---

$$\mathbf{v} = A^T \mathbf{u}$$

$$R^{-1} \mathbf{v} = \mathbf{i}$$

$$\mathbf{0} = A \mathbf{i}$$

$$\mathbf{0} = AR^{-1} A^T \mathbf{u}$$